



Höhere Technische Bundeslehranstalt Wels

4600 Wels, Fischergasse 30

ELECTROTECHNICAL LABORATORY

Title: **12. Resonance Circuit**

Date: 13.04.2017 / 20.04.2017

Author: Michael Gnadlinger

Group / Classname: A / 3AHME

Training supervisor:

Prof. Schwarzmüller

Team members:

Grüblinger Lukas

Gnadlinger Michael

Used instruments:

Gwinstek GDS-1022 824-30-229; W1.17-224 - oscilloscope

Fluke 177 True RMS W1.17-70

Fluke 177 True RMS W1.17-72

Fluke 177 True RMS W1.17-73

2x 1000 Ω plug-in resistor

coil with 1200 windings

capacitor with 4.7 μ F


Agilent U1732A W1.17-088 – CLR measuring instrument

Gwinstek AFG-2105 W1.17-326 – function generator

Remarks:

12.1 Series Resonance Circuit:

Preparation:

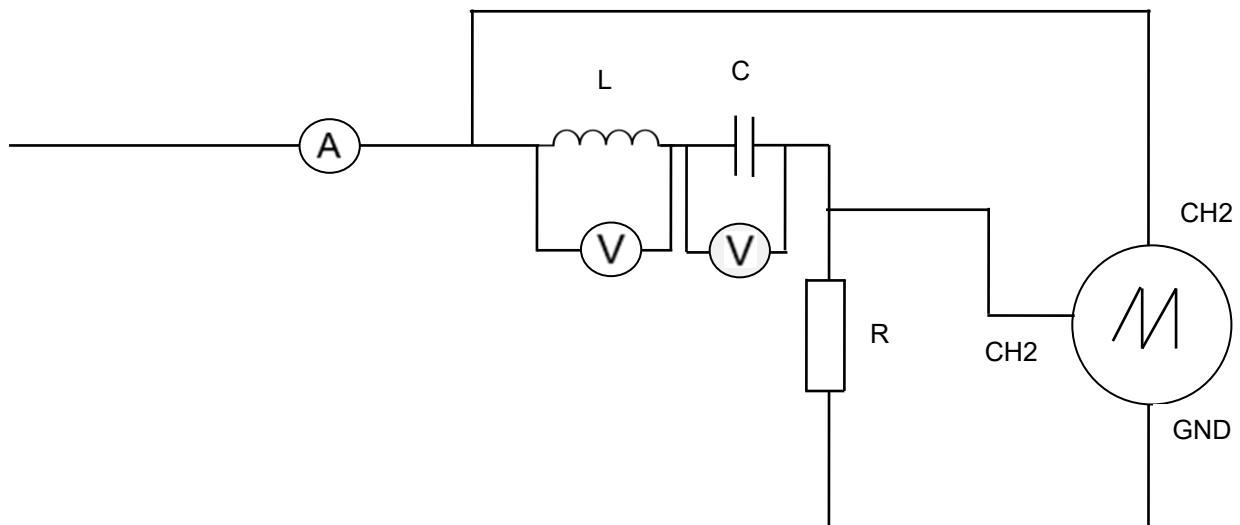

oscilloscope: Gwinstek GDS-1022 824-30-229; W1.17-224

V_L -Meter: Fluke 177 True RMS W1.17-73

V_C -Meter: Fluke 177 True RMS W1.17-70

A-Meter: Fluke 177 True RMS W1.17-72

R_m (R_{shunt}): 10 Ω -slider resistor

X_L : coil with 600 windings

$R = 505.8 \Omega$ (2x 1000 Ω in parallel)

$L = 5.414 \text{ mH}$ (400 windings)

$C = 4.773 \mu\text{F}$

|
- measured with Agilent U1732A W1.17-088
|

$$f_r = 1/[2*\pi*\sqrt{(L*C)}] = 990.07 \text{ Hz}$$

Ch1 = U_{ges}

Ch2 = I_{ges}

The task was to find a serial combination of a coil, a capacitor and a resistor to get a resonance circuit with a resonance frequency of around 1000Hz. Then supply it with a $V_{pp} = 3\text{V}$ sin-wave from a function generator and measure U_{ges} , U_c , U_L , I_{ges} , Z and phse shift φ over Δt . Therefore we needed to rise the frequency logarithmical from 0 to 10 kHz (max. frequency of the multimeters). At the end we had to further investigate behavior at the resonance frequency.


Measurement:

gegeben		gemessen				berechnet		Nebenrechnung	
[Hz]	[V]	[mV]	[mV]	[mA]	[μs]	[Ω]	[°]	[Ω]	[Ω]
f	U _{ges}	U _C	U _L	I _{ges}	Δt	Z	φ	Z _C	Z _L
1.58	3.00	17000.00	0.50	0.13	-156000.00	21110.96	-88.73	21104.95	0.05
2.51	3.00	2055.00	0.80	0.18	-96000.00	13294.73	-86.75	13285.19	0.09
3.98	3.00	2147.00	1.30	0.27	-60000.00	8393.47	-85.97	8378.35	0.14
6.31	3.00	2128.00	2.00	0.42	-37000.00	5308.54	-84.05	5284.60	0.21
10.00	3.00	2104.00	3.20	0.66	-23000.00	3372.39	-82.80	3334.58	0.34
15.85	3.00	2074.00	4.90	1.02	-13000.00	2163.26	-74.18	2103.84	0.54
25.12	3.00	1988.00	7.40	1.53	-7600.00	1419.76	-68.73	1327.46	0.85
39.81	3.00	1799.00	10.90	2.17	-3800.00	977.33	-54.46	837.62	1.35
63.10	3.00	1488.00	15.00	2.84	-2000.00	729.96	-45.43	528.46	2.15
100.00	3.00	1111.00	19.70	3.36	-880.00	603.96	-31.68	333.46	3.40
158.49	3.00	765.00	26.20	3.66	-340.00	545.77	-19.40	210.40	5.39
251.19	3.00	500.00	36.90	3.80	-132.00	520.83	-11.94	132.75	8.54
398.11	3.00	321.90	54.80	3.88	-29.00	510.65	-4.16	83.76	13.54
630.96	3.00	204.40	84.30	3.90	-14.00	506.77	-3.18	52.85	21.46
1000.00	3.00	128.30	130.70	3.90	0.00	505.80	0.00	33.35	34.02
1584.89	3.00	79.40	202.20	3.87	7.20	506.87	4.11	21.04	53.91
2511.89	3.00	47.60	305.80	3.80	9.20	510.92	8.32	13.28	85.44
3981.07	3.00	26.50	438.40	3.63	9.90	521.51	14.19	8.38	135.42
6309.57	3.00	12.40	568.40	3.27	9.90	547.41	22.49	5.28	214.63
10000.00	3.00	2.80	636.50	2.56	10.00	607.69	36.00	3.33	340.16

Calculation of the measurements:


$$\varphi = \Delta t / T * 360^\circ$$

$$|Z_{ges}| = \sqrt{(Z_C - Z_L)^2 + R^2}$$

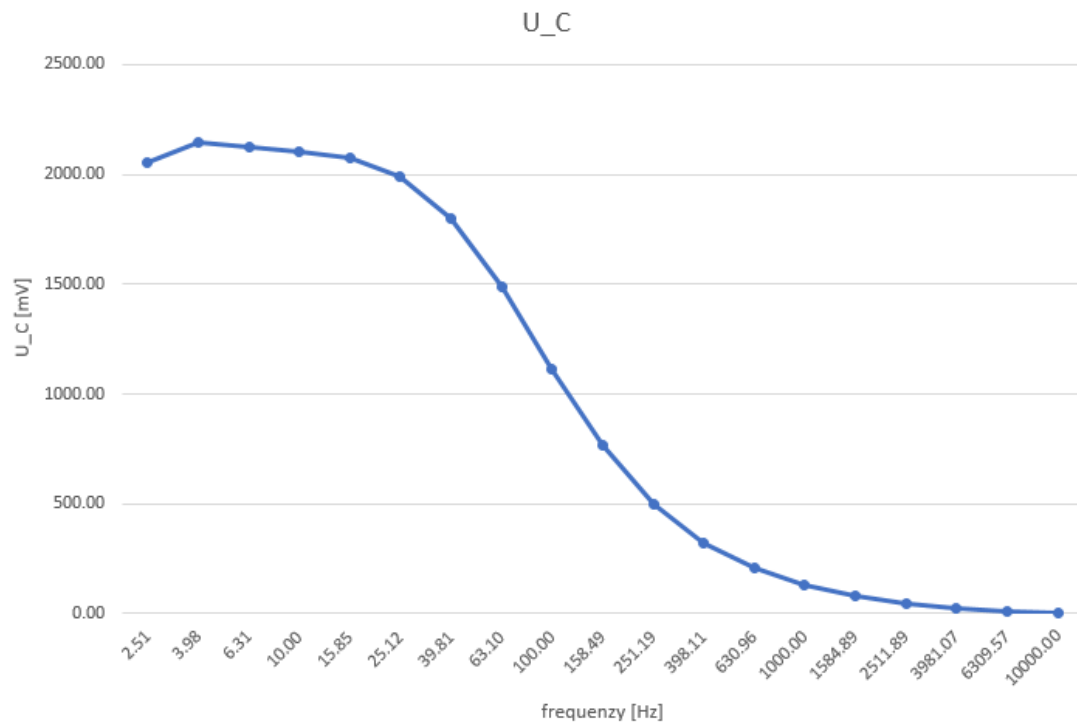

Conclusion:

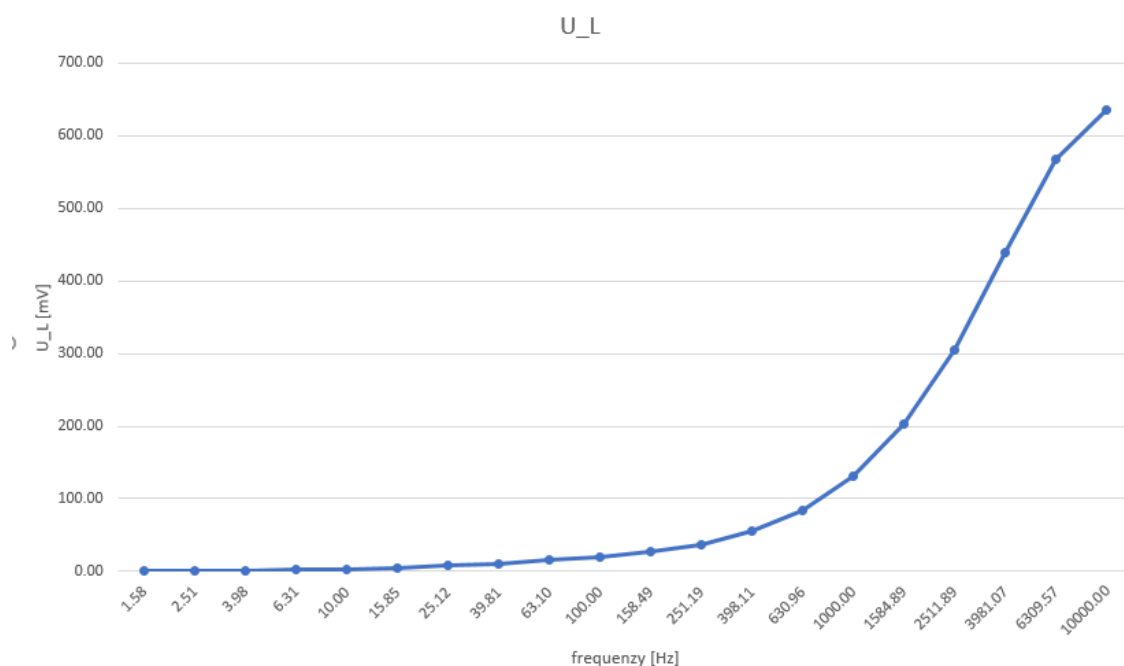
At low frequency the capacitor has a rather high resistance and therefore a higher voltage. This effect decreases when the frequency is increased.



Conclusion:


Other than the capacitor, the coil has a low resistance at a lower frequency and therefore a lower voltage, but a higher resistance when the frequency is increased.

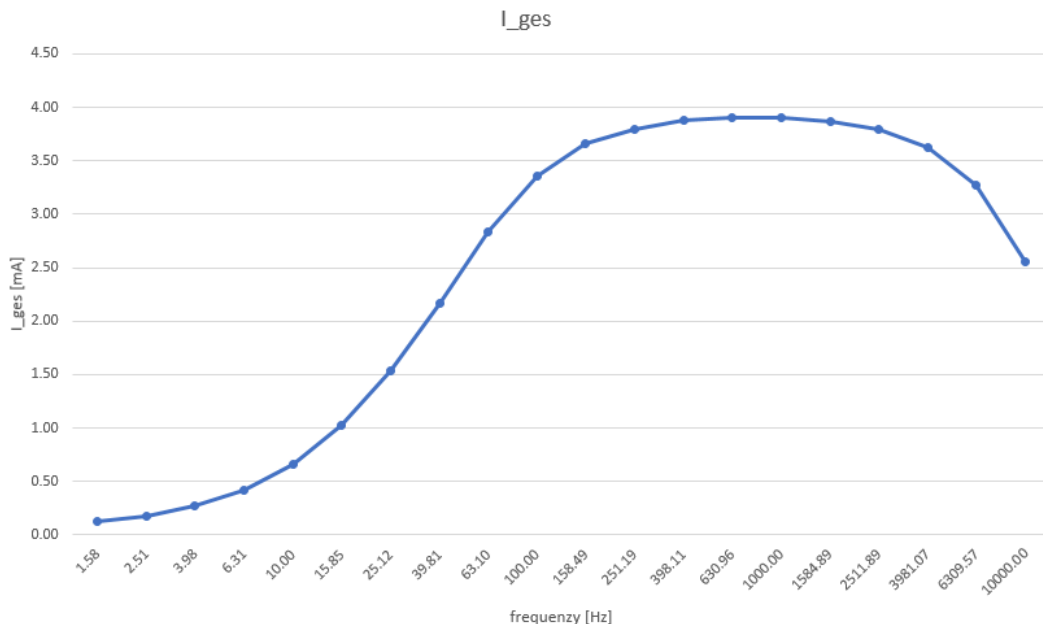You can also see, that at the resonance frequency, both components have approximately the same resistance and therefore the same voltage drop of around 130 mV (as seen in the table).



Conclusion:

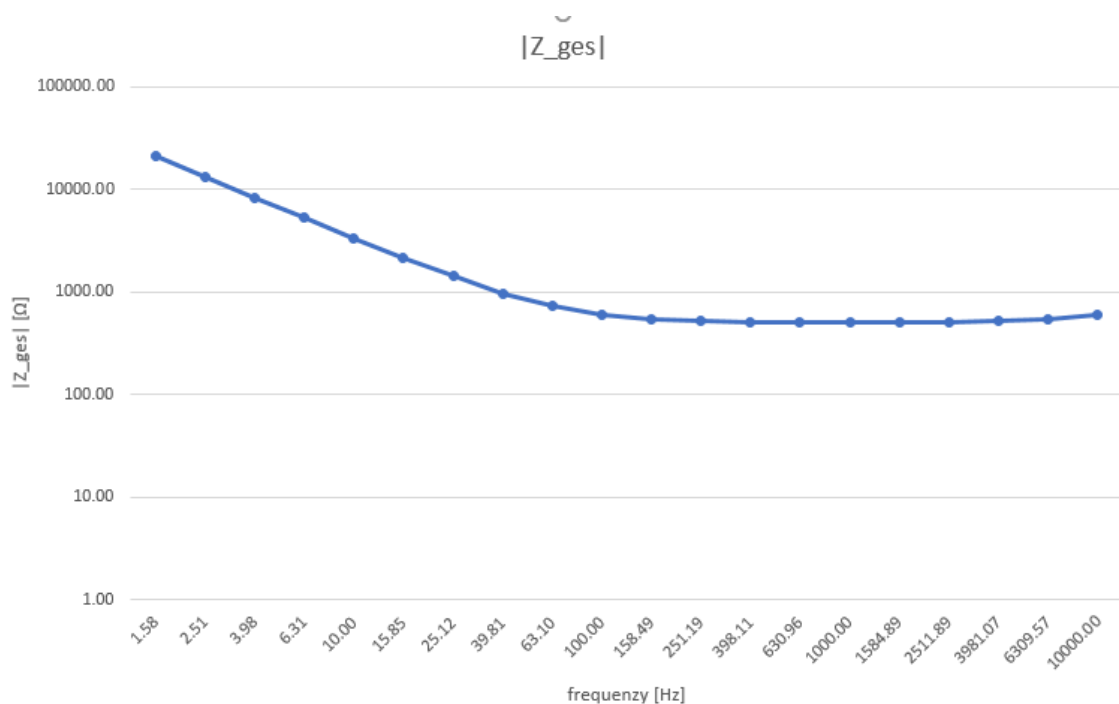
Because absolute value of the resistance of both compents is the same at the resonace frequency, but in the opposite direction of the imaginary-axis the left over resitance of our designed circuit is just the resistor R. This leads to a higher current than normal.



Conclusion:

Because the impedance of the coil doesn't increase at a higher frequency as much as the capacitor does at the lower frequency range and we used a rather big dampening resistor, the overall impedance at the resonace frequency isn't as segnificantly different than the impedance at the higher frequency. But it can still be seen that at 1000 Hz the only resistance of our circuete is just the 500 Ω dampening resistor.

phase shift [°]

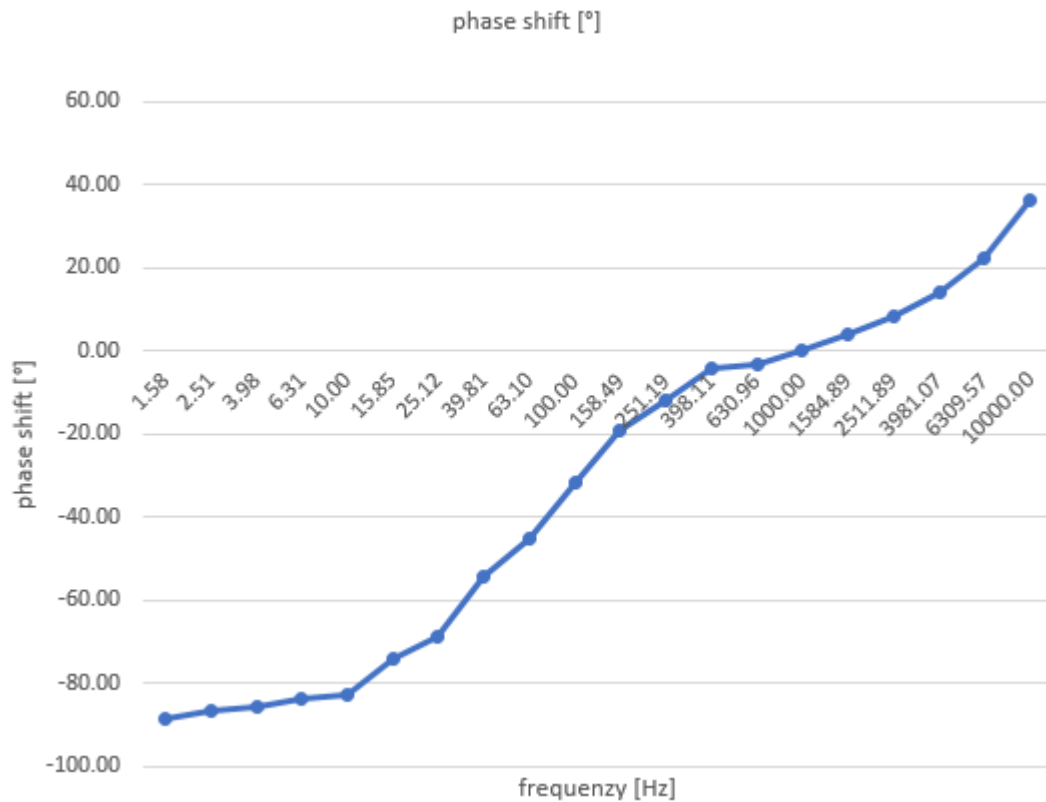


Conclusion:

I guess this diagram should look like a function 3rd grade with a saddle point at the resonance frequency which still can be seen. The cause of this bad graph may be a poor measuring job of us because to calculate the phase shift we needed to measure the time difference with the cursor function of the oscilloscope which can get a bit inaccurate.

12.2 Series Resonance Circuit:

Preparation:

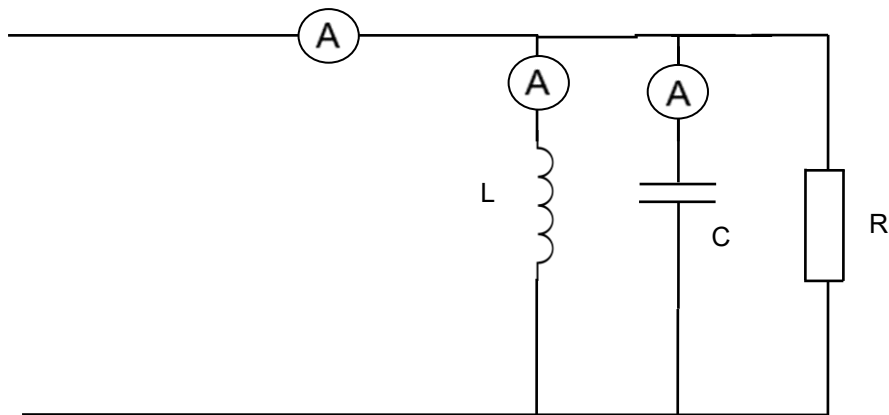

A_L -Meter: Fluke 177 True RMS W1.17-73

A_C -Meter: Fluke 177 True RMS W1.17-72

A -Meter: Fluke 177 True RMS W1.17-70

We used the same components as for task 12.1 and therefore got the same resonance frequency of about 1000 Hz.

Also the supplied voltage was still 3V out of the same function generator and increasing the frequency logarithmical.

For this task only the currents at the coil, the capacitor and the overall circuit has to be measured simply using multimeters. Then the impedance in dependence of the frequency has to be calculated.


Measurements:

gegeben		gemessen			berechnet		Nebenrechnung	
[Hz]	[V]	[mA]	[mA]	[mA]	[Ω]	[°]	[Ω]	[Ω]
f	U_ges	I_ges	I_L	I_C	Z	φ	Y_C	Y_L
1.58	3.00	42.39	42.08	0.08	0.05	4.21354202	0.00	18.61
2.51	3.00	43.24	42.50	0.08	0.09	2.65306069	0.00	11.71
3.98	3.00	40.78	40.07	0.08	0.14	1.67332516	0.00	7.39
6.31	3.00	37.93	37.31	0.09	0.21	1.05546059	0.00	4.66
10.00	3.00	36.73	36.26	0.11	0.34	0.66596608	0.00	2.94
15.85	3.00	36.67	36.22	0.14	0.54	0.4201059	0.00	1.85
25.12	3.00	36.81	36.38	0.21	0.86	0.26497277	0.00	1.17
39.81	3.00	36.88	36.48	0.32	1.36	0.16703448	0.00	0.74
63.10	3.00	36.88	36.57	0.51	2.16	0.10512458	0.00	0.47
100.00	3.00	36.81	36.70	0.84	3.44	0.06592471	0.00	0.29
158.49	3.00	36.59	37.01	1.53	5.53	0.04094737	0.00	0.19
251.19	3.00	35.97	37.76	3.08	9.13	0.02480878	0.01	0.12
398.11	3.00	34.18	39.58	7.07	16.15	0.01402521	0.01	0.07
630.96	3.00	28.27	43.50	18.24	36.05	0.00626907	0.02	0.05
1000.00	3.00	14.62	41.29	42.12	484.61	0.00013389	0.03	0.03
1584.89	3.00	30.42	18.94	47.66	34.43	0.00656578	0.05	0.02
2511.89	3.00	36.45	6.87	42.66	15.71	0.01441499	0.08	0.01
3981.07	3.00	37.23	2.59	39.41	8.93	0.02537559	0.12	0.01
6309.57	3.00	35.77	0.95	36.44	5.42	0.04181354	0.19	0.00
10000.00	3.00	32.08	0.20	32.20	3.37	0.06727701	0.30	0.00

Calculation of the measurements:


$$\varphi = \arctan \left(\frac{Y_C - Y_L}{R} \right)$$

$$|Z_{ges}| = \left| \sqrt{(Z_C - Z_L)^2 + R^2} \right|$$

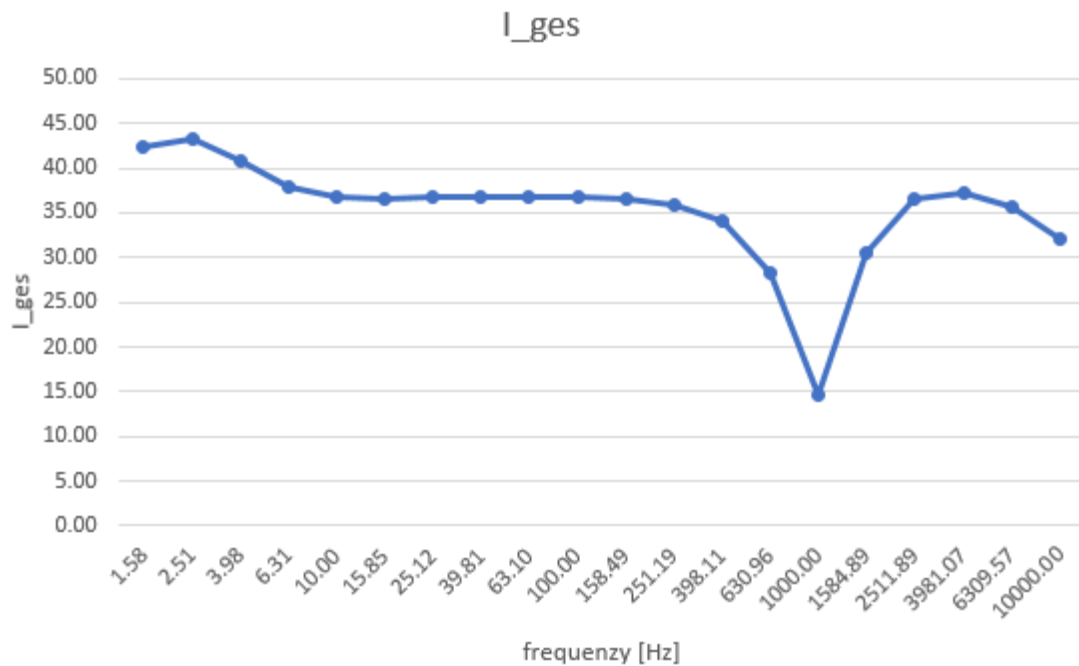


Conclusion:

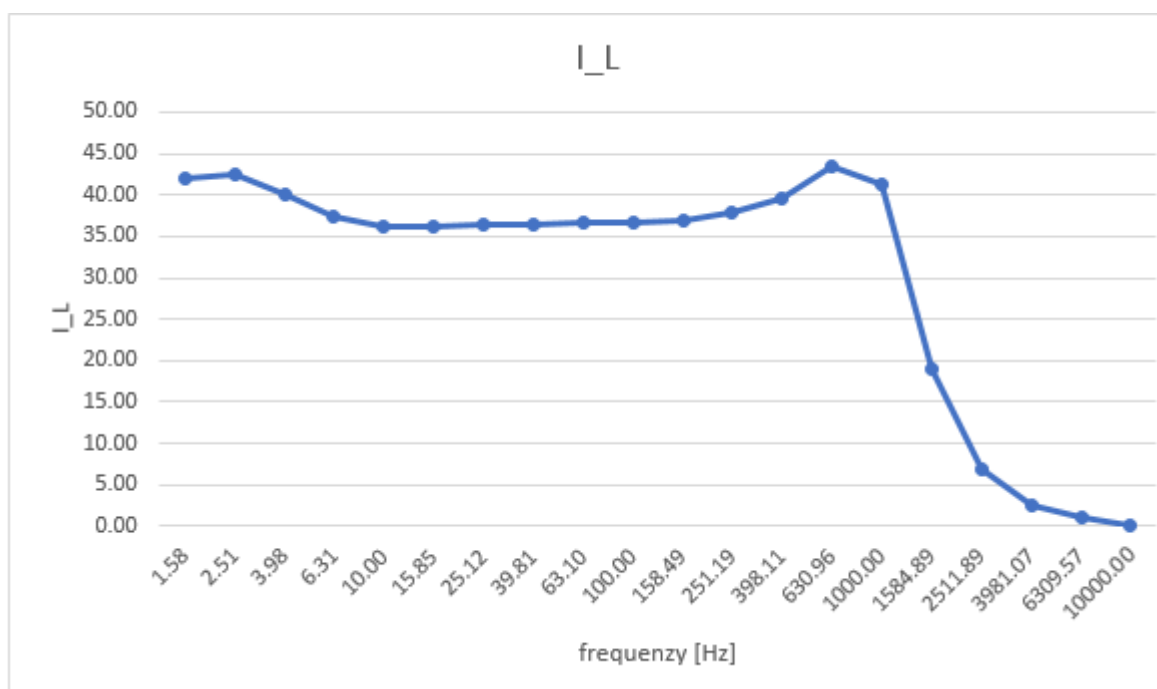As typical for a parallel resonance circuit the overall resistance increases heavily at the resonance frequency, other than the serial circuit, and therefore lowers the overall current it draws.



Conclusion:

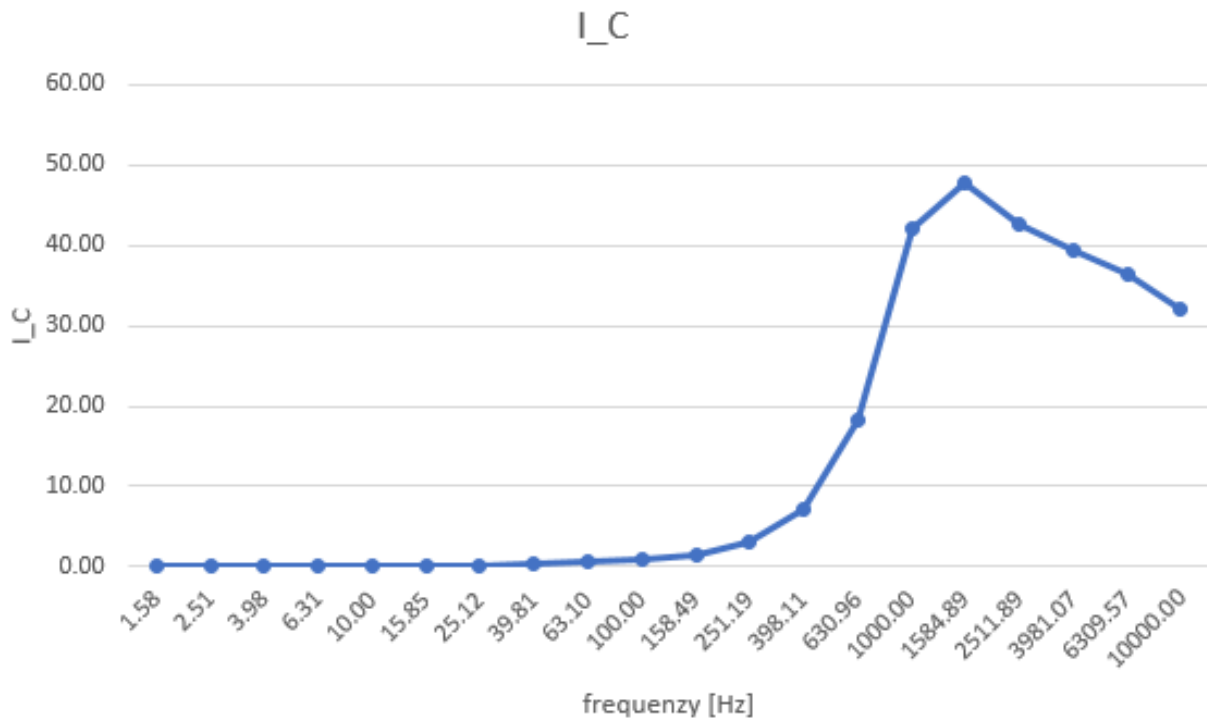
It can clearly be seen that the admittance of a coil decreases with an increasing frequency, which ultimately means a higher impedance. But it is interesting to see that this effect just significantly affects the current draw after the resonance frequency. This may be better explained with the next diagram.



Conclusion:

On the one hand the capacitor has a very high impedance at the lower frequency range which means that it heavily affects the current flow and almost allows no current to pass through the capacitor. On the other hand we used a fairly high resistor R of around $500\ \Omega$. Ultimately this means that as long as the capacitor doesn't draw significantly more current than the coil increases its impedance with the frequency almost all of the current will flow through it, with only little effect of the frequency.

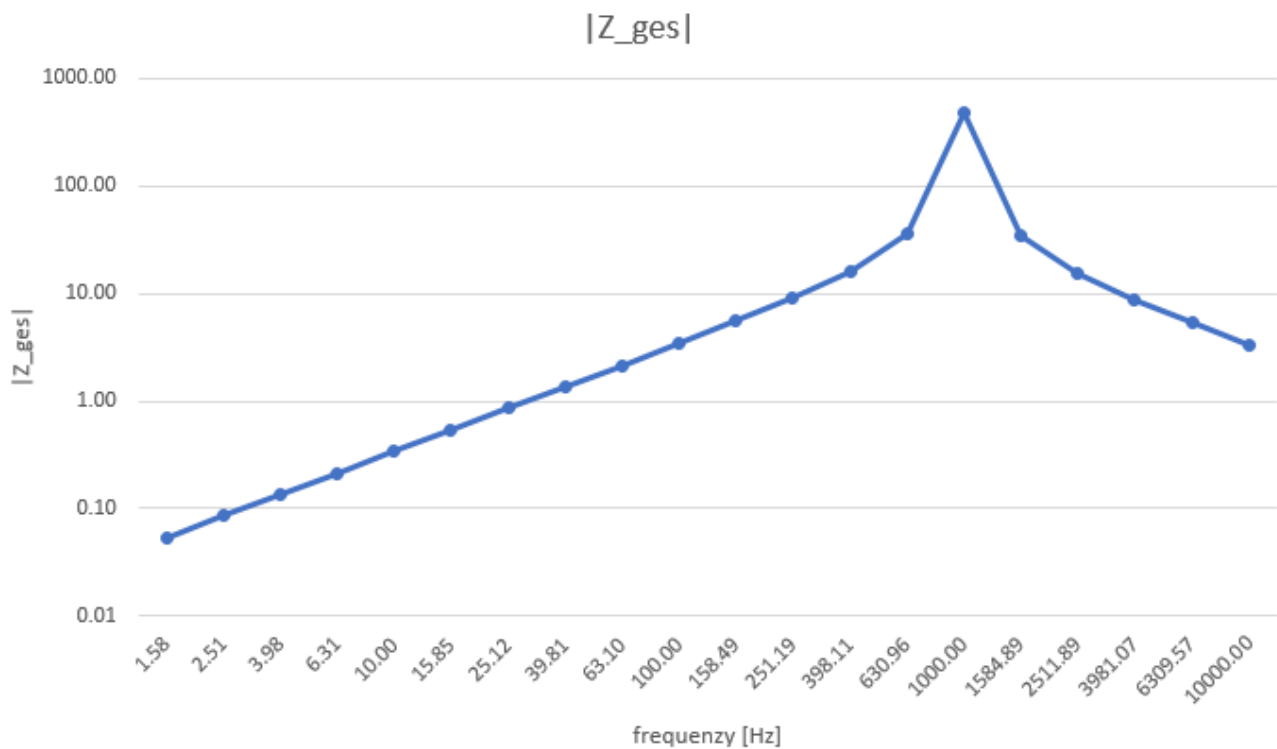In this diagram it can be observed that the capacitor's impedance decreases with the frequency.



Conclusion:

Due to the logarithmical scale of the impedance it seems to increase linear but only by a little bit. This keeps going until near the resonance frequency where the overall impedance peaks out to decrease again. This peak is because the impedances of the coil and the capacitor are of the same absolute value but in opposite directions which means the impedance is theoretically just covered by the resistor R . In our setup we didn't quite get this result: the impedance at the resonance frequency was 484.61 Ω .